

*Date:* \_\_\_\_\_


*Student:* \_\_\_\_\_

Design a 16-segment decoder using PLDs. It must decode as a minimum the 26 letters of the alphabet (A  $\rightarrow$  Z) and the 10 digits (0  $\rightarrow$  9). Use two 22V10 since a 22V10 provides only 10 outputs.



Information to help in this design is attached on the next slides:

- 22V10 pin out
- 16 segment display naming convention
- 16 segment display pin numbering scheme
- An example of possible codes to use


# 22v10 – Pin Diagram

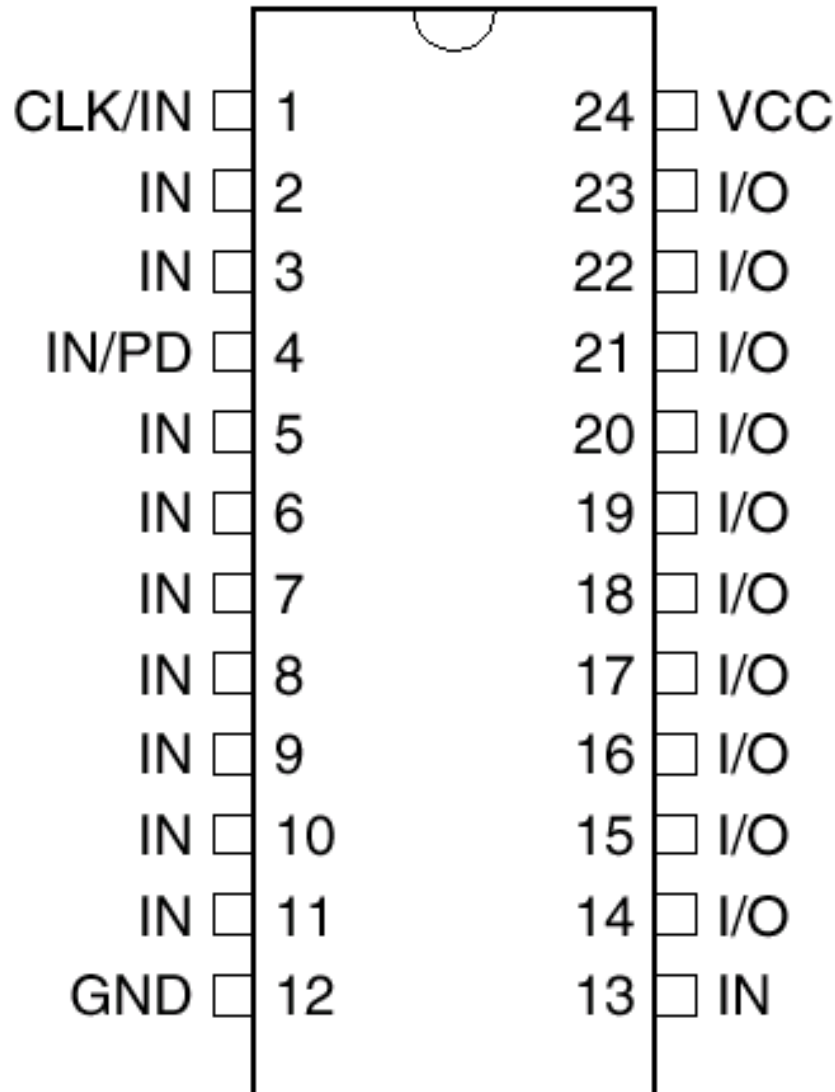

## FYS-15012Bx

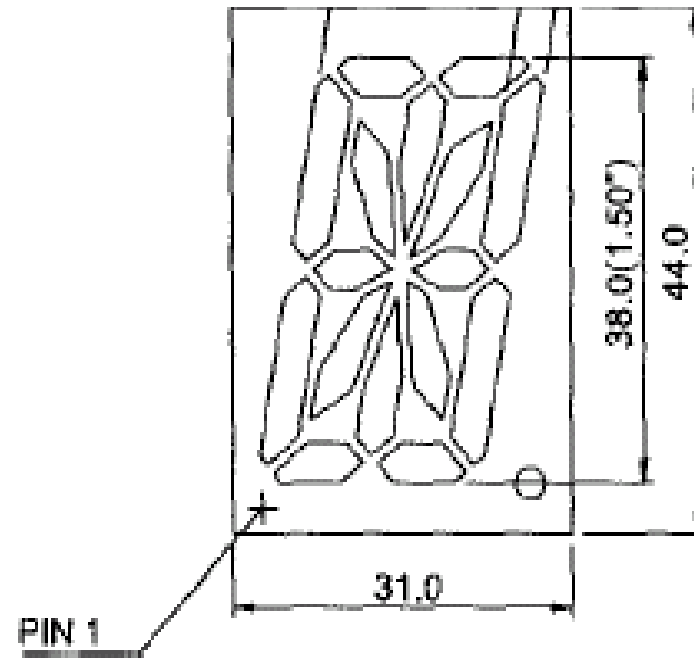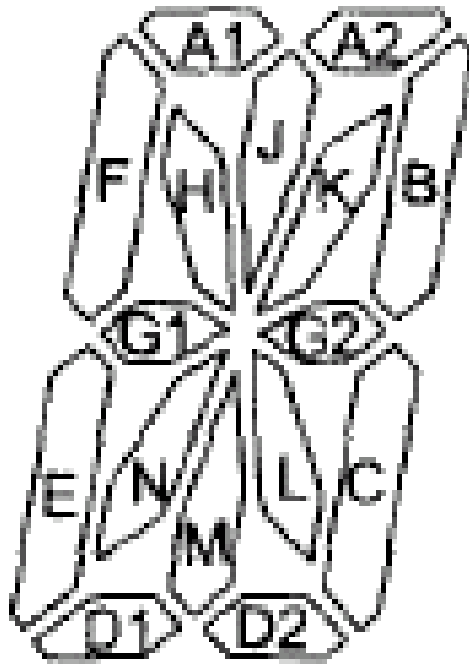

## FYS-15012Bx

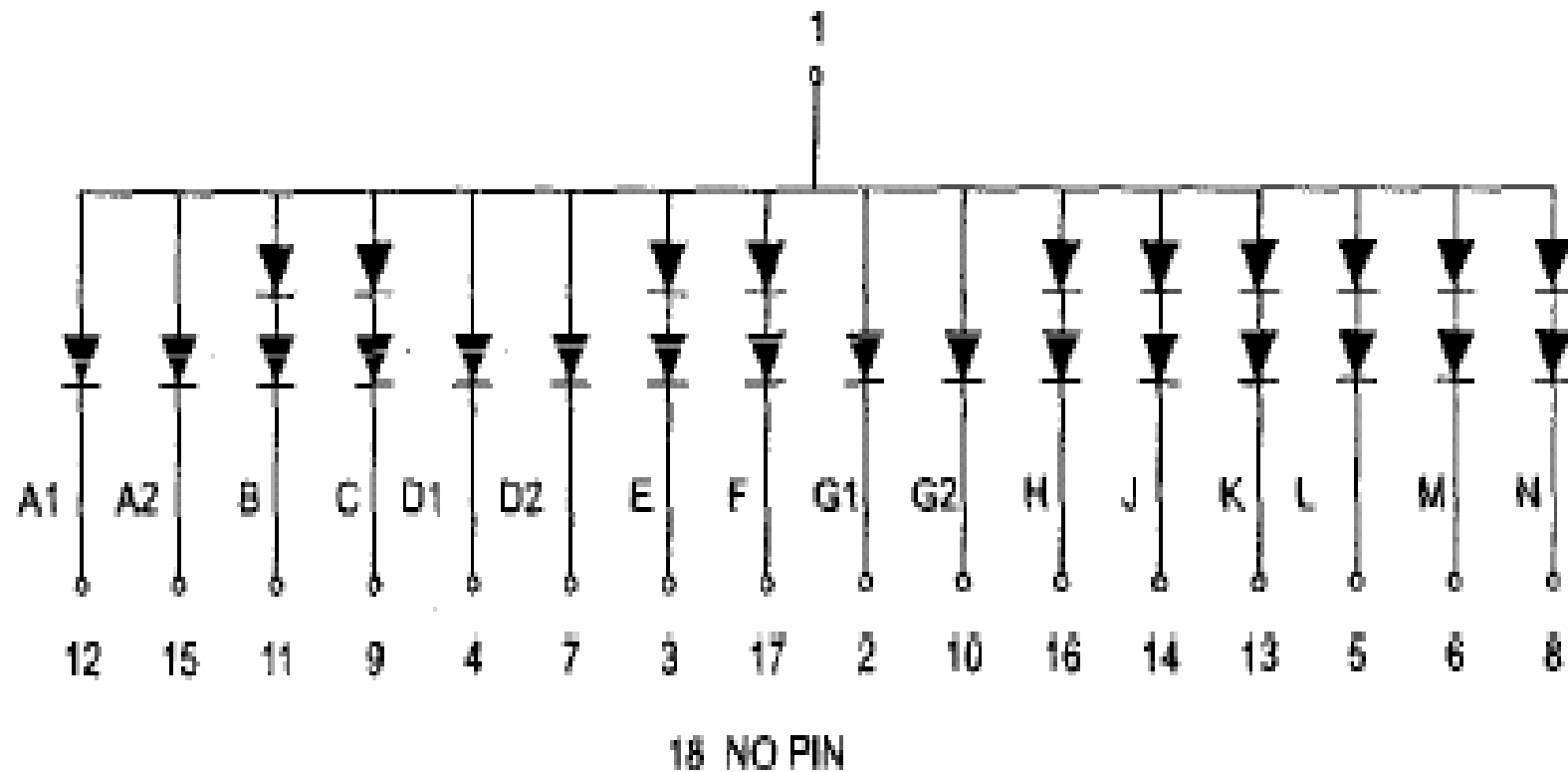

## A possible decoding solution

### Character Set

BITS		D <sub>3</sub>	0	0	0	0	0	0	0	0	1	1	1	1	1	1	1
		D <sub>2</sub>	0	0	0	0	1	1	1	1	0	0	0	0	1	1	1
		D <sub>1</sub>	0	0	1	1	0	0	1	1	0	0	1	1	0	0	1
		D <sub>0</sub>	0	1	0	1	0	1	0	1	0	1	0	1	0	1	1
D <sub>6</sub> D <sub>5</sub> D <sub>4</sub>	HEX	0	1	2	3	4	5	6	7	8	9	A	B	C	D	E	F
0 1 0	2	(space)	!	"	#	\$	%	&	'	<	>	*	+	,	-	.	/
0 1 1	3	0	1	2	3	4	5	6	7	8	9	=	/	<	=	>	?
1 0 0	4	a	A	B	C	D	E	F	G	H	I	J	K	L	M	N	O
1 0 1	5	P	Q	R	S	T	U	V	W	X	Y	Z	[	\	]	^	_