

# Toll Collector FSM Design Individual Project

# ***LAB PROJECT: Toll Collector FSM***

## Requirements

- ☐ Design an FSM to accept 15 Cents using either Nickels ( $N = 0/1$ ) or Dimes ( $D = 0/1$ ). Accept money above 15 cents with no change.
- ☐ Two Push button switches are used to simulate the Nickel and Dime coins.
- ☐ A PLD is used to implement the FSM
- ☐ Two 7-segment displays shows the amount of money entered: (00, 05, 10, 15). Remain at 15 if money  $> 15$  cents.
- ☐ LEDs are used to notify the driver when to stop (RED) & go (GREEN)
- ☐ A push button is used to reset the FSM (Display 00, Red light turned ON)
- ☐ Power is to be provided by a 9 volt battery
- ☐ Clocking is generated using a 555 timer chip

## Main components

1. PLD
2. two 7-segment displays
3. Red LED
4. Green LED
5. 7805 voltage regulator
6. 555 timer chip
7. Three push button switches

Student Name: \_\_\_\_\_

Grade: \_\_\_\_\_ / 100

## Toll Collector Project

Item	Weight	Points
Simulation	10%	
Nickel Detection	10%	
Dime Detection	10%	
Red STOP Light	10%	
Green GO Light	10%	
7-segment display (2)	20%	
Reliability	10%	
9 volt battery operated	10%	
555 clock generation	10%	

Total Grade: